

Simple Echo Chamber

By PETER F. BRETHERICK

ONE OF THE MODERN EFFECTS USED BY RECORDING organisations is the addition of echo, and it plays a major part in the recording of "pop" records today. The echo effect is introduced by the use of what is called an "echo chamber" and, although its name implies that it is a large hollow container, it can in practice be a small electric device which is sometimes no bigger than a shoe-box.

It may be thought by the reader that the echo effect would require either a colossal concrete funnel or a complex tape mechanism which would be too complicated and too expensive for the average constructor. The unit about to be described has none of these disadvantages. It can be employed with almost any type of microphone or electric guitar and quite amusing results can be obtained when it is used with a radio tuner.

Basically, the unit consists of a high gain amplifier with a power output of some 3 to 4 watts (which is in excess of that necessary), together with an echo coil and a pick-up. The amplifier drives a small loudspeaker to which the echo coil is coupled. The audio signal from the loudspeaker travels down the coil and, after a delay in time, reaches the other end where it is detected by the pick-up and fed, together with the normal signal from the output of the echo amplifier, to the main amplifier. Thus, the main amplifier which, in the case of a guitar, would be the guitar amplifier, receives the normal signal and the echo signal via one lead. See Fig. 1.



The Echo Amplifier

The echo amplifier, the circuit of which is shown in Fig. 2, consists of a directly coupled triode-pentode valve, ECL82, fed from an EF86 high gain voltage amplifying pentode. Any other suitable amplifier could, of course, be used, provided that it has a high gain and adequate power output. It should be noted that excessive output power would result in distortion from the small speaker employed, and would also tend to make the echo coil jump about somewhat.

The amplifier is designed primarily for simplicity and low hum level. Consequently, all component values are critical and all input connections must be screened. The h.t. supply must be provided by a double-wound mains transformer as, quite apart from safety reasons, the unit will be used in conjunction with a high power amplifier whose chassis is almost sure to be earthed. The 10-watt resistor, R_9 , should be kept reasonably clear of the other components due to its dissipated heat which, although not excessive, is quite considerable. The layout is not critical, except that all leads should be as short as possible and heater leads tightly twisted and kept close to the chassis. An 18 s.w.g. aluminium chassis approximately 8 x 6 x 2½ in will be found suitable.

The circuit should need little explanation, the only unusual thing being the relatively low values of the coupling capacitor C_3 , and the bass cut capacitor, C_1 , in the guitar input channel. The aim of both these components is to cut the bass frequencies as much as possible, in order to compensate for the loss of treble in the echo coil.¹

The Echo Coil

Initially, the reader may have visions of this coil consisting of yards of wire draped all around the room. However, if it is wound carefully and suspended properly, it should stretch out to no more than 24 inches.

¹ C_6 , in conjunction with VR_2 , forms a bass boost control. Whilst it may seem rather surprising to boost the bass after it has been cut, the circuit is, in practice, more straightforward than other forms of tone control.

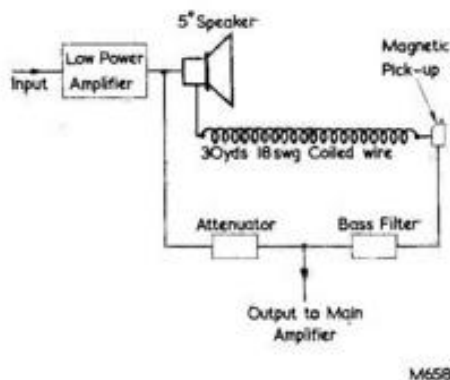


Fig. 1. The basic principles of the echo unit

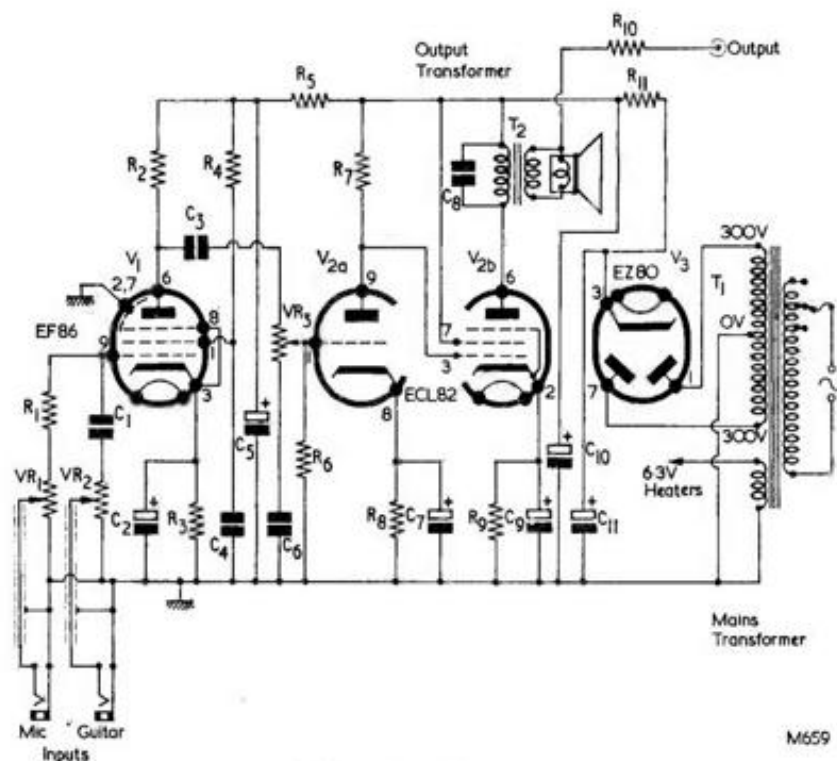


Fig. 2. The circuit of the echo amplifier

Components List (Fig. 2)

Resistors

R ₁	100kΩ	½ watt	20%
R ₂	100kΩ	½ watt	Hi-Stab
R ₃	2.2kΩ	½ watt	Hi-Stab
R ₄	390kΩ	½ watt	Hi-Stab
R ₅	100kΩ	½ watt	20%
R ₆	1MΩ	½ watt	20%
R ₇	470kΩ	½ watt	20%
R ₈	2.2kΩ	½ watt	5%
R ₉	2.7kΩ	10 watt	5%
R ₁₀	1MΩ	½ watt	20%
R ₁₁	470Ω	1 watt	20%
VR ₁	1MΩ	log	
VR ₂	1MΩ	log	
VR ₃	1MΩ	log	

Capacitors

C ₁	0.005μF	350 w.v.
C ₂	50μF	electrolytic, 12 w.v.
C ₃	0.01μF	350 w.v.
C ₄	0.25μF	350 w.v.
C ₅	16μF	electrolytic, 350 w.v.
C ₆	400pF	350 w.v.
C ₇	50μF	electrolytic, 12 w.v.
C ₈	0.01μF	350 w.v.
C ₉	16μF	electrolytic, 150 w.v.
C ₁₀	32μF	electrolytic, 350 w.v.
C ₁₁	32μF	electrolytic, 350 w.v.

Valves

V ₁	EF86
V ₂	ECL82
V ₃	EZ80 or EZ81

Miscellaneous

T ₁	Primary to suit mains voltage. Sec: 300-0-300V 60mA, 6.3V 2A.
T ₂	55:1 for 3Ω speaker
B9A	valveholders (3), chassis
8 x 6 x 2½ in.	5 in speaker (see text)

18 s.w.g. galvanised iron wire was found to be the best and the cheapest material for the coil, and this is obtainable from most hardware merchants in 50-yard coils for a few pence. Copper wire, which would need only two-thirds the length to produce the same time-lag of echo, was found to be very flimsy and needed more support; it was also considerably more expensive.

The coil should be wound on a 1 in diameter former, e.g. a broom-stick, using about 30 yards of the wire. It must be carefully wound, each turn touching its predecessor. When the finished coil, which should take about 30 minutes to wind, is carefully pulled off the former, it should stretch

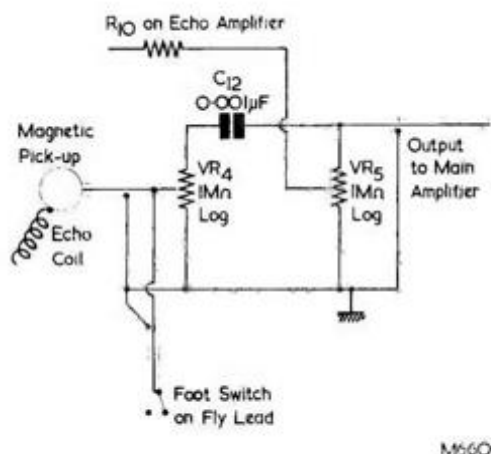


Fig. 3. The output mixing controls

Components List

(Fig. 3)

Potentiometers

VR₄ 1MΩ Log

VR₅ 1MΩ Log

Capacitor

C₁₂ 0.001µF, 350 w.v.

Pick-Up

Magnetic (see text)

Switch

Foot-switch. Open when depressed

a maximum of 36 inches when held vertically and no turns should be touching. The 1in diameter former was used as it gave the best result for length and needed little support.

The Pick-Up

The most effective detection device was found to be a magnetic pick-up of the type found in old 78 r.p.m. record players and which are readily obtainable on the surplus market, if not already to hand. The end of the coil should neatly clamp in the needle socket in the pick-up.

A headphone could be used as a magnetic microphone, having its diaphragm drilled and the end of the coil pushed through and bent over. The only drawback to this is that acoustic feedback occurs if the volume is turned too high. There is, of course, no reason why a crystal pick-up should not be used, provided the reader can devise a method of connecting the end of the coil to it. Whichever method is used, the impedance must be fairly high; if a low impedance pick-up is used, a matching transformer must be employed.

The Output Controls

Fig. 3 shows how the echo and the main signal

are mixed. Tone compensation for the echo output is again provided by means of the 0.001µF capacitor. A foot switch is provided to turn the echo on or off, as required. Except, of course, for the pick-up, foot-switch and output lead, the components shown in Fig. 3 should be mounted on the same chassis as the amplifier. There should now be five controls on the amplifier, giving a wide variety of effects.²

Assembly

The choice of case is left to the constructor, but it was found that a cabinet 24 x 8 x 7in successfully housed everything. The amplifier and speaker should be mounted at one end of the cabinet and the pick-up at the other. The speaker should be chosen with care, for it must have a tough cone. The free end of the coil, i.e. the opposite end to the pick-up, should now be carefully pushed through the cone and bent in a right angle behind it. The coil should be supported where necessary by means of elastic held by drawing pins at the top and bottom of the cabinet. If the coil is too long for the cabinet it may be doubled back. See Fig. 4.

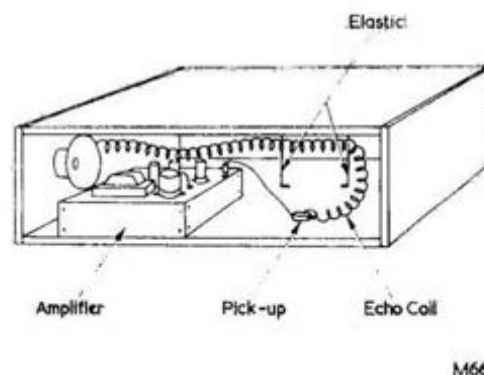


Fig. 4. Internal layout of the "echo chamber"

Finally

Should the echo produced be very distorted, the coil should be checked to see if any turns are touching or whether the coil touches the sides of the cabinet. If it is touched or gently flicked with the main amplifier switched on, a loud clang should result from the main amplifier. If this does not happen, check that the pick-up is working and that the associated connections are correct; also make sure that the foot switch is not in the closed position.

² It will be noted that, as with VR₁ and VR₂ of Fig. 2, the inputs to the potentiometers in Fig. 3 are applied to the sliders instead of across the tracks, as is more usual. This method of connection ensures that one level is not unduly affected by adjustments in the other potentiometer.